



CIS009-2, MECHATRONICS SIGNALS & MOTORS

David Goodwin

Department of Computer Science and Technology
University of Bedfordshire

13th December 2012



Outline

Mechatronics

David Goodwin

Digital signals
Information encoding
Digital to analogue conversion
Analogue to digital conversion
Computers
DC motors
DC motor loading
Stepper motor

- 1 Digital signals
- 2 Information encoding
- 3 Digital to analogue conversion
- 4 Analogue to digital conversion
- 5 Computers
- 6 DC motors
- 7 DC motor loading
- 8 Stepper motor



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

3

DIGITAL SIGNALS

52



Signals

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor



Department of
Computer Science and
Technology
University of
Bedfordshire

4

- Two types of signals exist:

Analogue signal In an analogue signal voltages and currents continuously change with time.

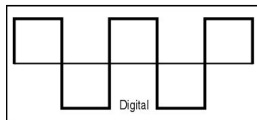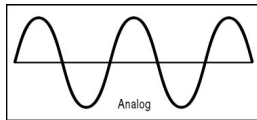Digital signal In a digital signal voltages are switched on and off. Thus, the signal consists of a train of pulses.



52



Digital Signal

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion



Computers

DC motors

DC motor loading

Stepper motor

5

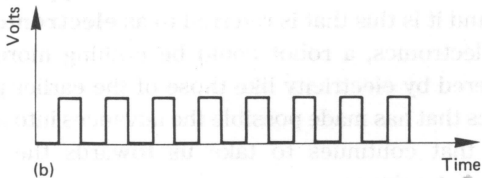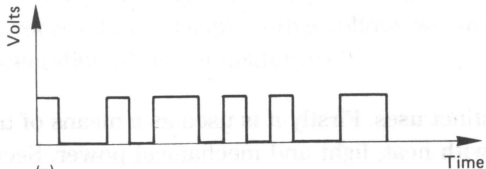

- (a) A digital signal containing information
- (b) Timing pulses produced a clock used for distinguishing



Transmission of digital signals

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading


Stepper motor

6

- Two methods are used:

Parallel transmission Uses several wires in parallel to carry the electrical signal corresponding to a different bit in the message.

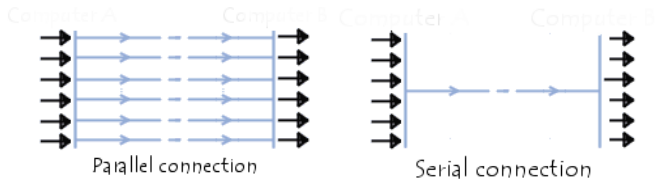Serial transmission Individual bits which constitute the information can be sent one by one, down a single pair of wires.





Mechatronics

David Goodwin

Digital signals

Information encoding

7

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

INFORMATION ENCODING

Department of
Computer Science and
Technology
University of
Bedfordshire

52



Encoding information

Mechatronics

David Goodwin

Digital signals

Information encoding

8

Digital to analogue conversion

Analogue to digital conversion

Computers

DC motors

DC motor loading

Stepper motor

- We use a simple example to illustrate how information can be encoded in digital format.
- For example we could encode temperature information using 2 bits as:
 - 1, 1 Very hot (i.e.two pulses in succession).
 - 1, 0 Hot (i.e.a pulse followed by a space).
 - 0, 1 Warm (i.e. a space followed by a pulse).
 - 0, 0 Cold (i.e. two spaces in succession).
- NOTE: Using 4 bits will allow the temperature to be represented to 16 levels



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

9

DIGITAL TO ANALOGUE CONVERSION

52



Digital circuits

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

10

- These use or produce digital signals. Three categories exist:
 - Logic circuits** Circuits with digital signals as both inputs and outputs
 - Analogue-Digital Converter (ADC)** This has an analogue input and a digital output.
 - Digital-Analogue Converter (DAC)** This has a digital input and an analogue output.

52



Digital-Analogue Converter (DAC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

11

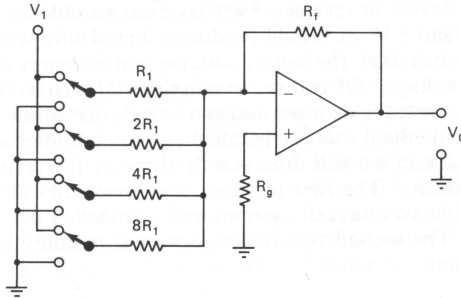

$$\text{A 4-bit D/A converter now, } V_0 = -\frac{V_1 R_f}{R_1} \left[X_1 + \frac{X_2}{2} + \frac{X_3}{4} + \frac{X_4}{8} \right]$$

- Note that the resistors are in the ratio of 2^0 , 2^1 , 2^2 and 2^3 . It is difficult to fabricate these array of resistors on a single chip therefore the following alternative is preferred.



Digital-Analogue Converter (DAC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

12

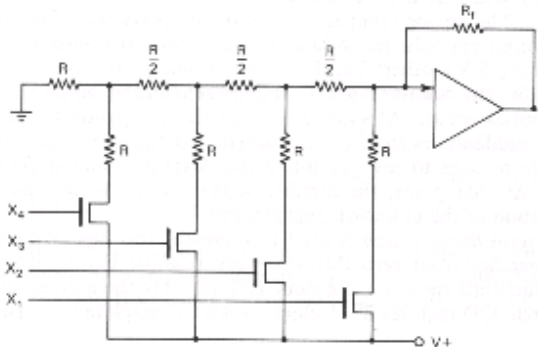

$R - 2R$ implementation of a D/A converter.

- Commercial implementation of DAC. Note that the switches in previous diagram have been realised with field effect transistors



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

13

ANALOGUE TO DIGITAL CONVERSION

52



Steps in converting analogue

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

14

- signals to digital form
 - Sample the analogue signal at regular short intervals.
 - The sampled signals are coded using binary digits.
 - In practice we need a digital to analogue converter to implement it.



Analogue-Digital Converter (ADC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

15

- Three types exist:

Linear search converter The simplest of all A-D converters.

Successive approximation converter

Flash converter The fastest method to encode an analogue signal to a digital form.

52



Linear Search Converter (ADC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

16

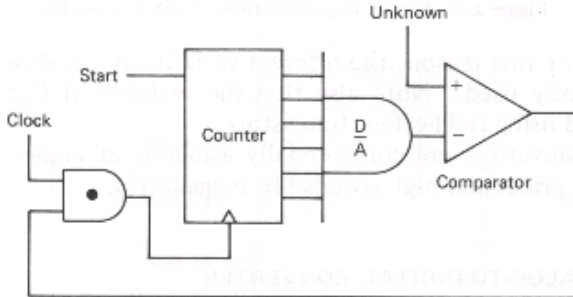

A simple A/D converter.

- It consists of a Counter, D-A, Comparator and NAND gate



Linear Search Converter

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

Department of
Computer Science and
Technology
University of
Bedfordshire

17

- How it works:

- The analogue comparator has the property that if the voltage on the + input is greater than voltage on the - input the output is binary "1" (typically 5V) otherwise "0" (typically 0V). The sequence of operation is as follows:
 - 1 Set the counter to zero
 - 2 Apply signal to be converted at the unknown terminal
 - 3 Start counter. The D-A converts the counting sequence into volts
 - 4 If the - input is greater than + input, the comparator output becomes zero disabling the AND gate and stopping the counter. The number in the counter is the best approximation.

52



Successive Approximation Converter (ADC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


18

Computers

DC motors

DC motor loading

Stepper motor

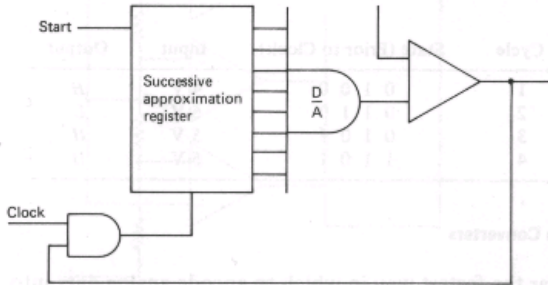

Successive approximation A/D converter.

- This is the same as the Linear search technique except that counter is replaced with a Successive Approximation register.



Algorithm for successive approximation (ADC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion

Computers

DC motors

DC motor loading

Stepper motor

19

- 1 Let the variable M represent the most significant bit.
- 2 Set M bit to 1
- 3 If the D-A output exceeds the unknown, set the M bit to 0
- 4 Let the variable M represent the next most significant bit.
- 5 If all bits have been checked stop; also go to 2.



Flash Converter (ADC)

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

20

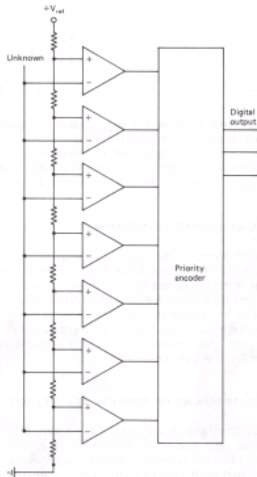

A 3-bit flash encoder.

- A resistive divider network of 2^n resistors divide the reference voltage into many equal increments.
- The unknown is applied inputs exceeding the unknown are on,; all others are off.
- The comparator code is is converted to a binary code by the priority encoder



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

21

COMPUTERS

52



Microprocessor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

22

- Microprocessors, logic gates, A-D and D-A are parts of robotic systems.
- Microprocessor and logic gates are studied in Computer Systems Architecture and will not be discussed here.
- Both A-D and D-A are interfaces of robotics system to the real world.

52



Computers used in automation

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

23

Mainframes Large computer with large word length (> 32 bits).

Mini-computers

Microcomputers

Programmable logic controllers This are computers dedicated for control purposes.



Programmable logic controller

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

24

- Responds to sensors
- Can make decisions about the sensors according what it is programmed to do.
- Can be programmed to simulate PI, PD and PID controllers.
- Some control applications of PLC are:
 - Industrial equipment such as motors, pumps and valves, Furnaces, packaging machinery.

52



Bus systems

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

25

- All computers make use of address, data and control bus systems as summarised below:
 - Address bus is used to carry the address of memory locations.
 - Data bus is used to carry the computer word, The larger the data bus the more powerful the computer is.
 - Control bus carries control signals such as READ/WRITE, INTERRUPT etc, signals.



I/O management

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

26

- Memory mapped I/O
- Isolated I/O Addressing
- Input/Output Ports
- Parallel I/O Ports
- Programmable I/O Ports

52



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

27

DC MOTORS

52



Electric motors

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

28

- Three basic characteristics of electric motors are:
 - Power
 - Torque
 - Speed

52



Power

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

29

- One can distinguish between two types of power
Electrical power A measure of electricity used by the motor.
Mechanical power The power (work) produced by the motor. Measurement of Power (in Watts).
1hp=745.7Watts.



Torque


Mechatronics

David Goodwin

Digital signals
Information encoding
Digital to analogue conversion
Analogue to digital conversion
Computers
DC motors
DC motor loading
Stepper motor

30

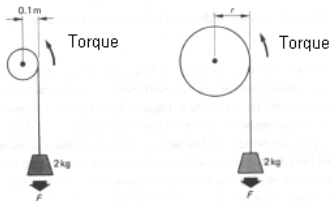- This is the turning force a motor is able to produce. The force multiplied by the shortest distance measured from the axis of rotation to the line along which the force acts. It is measured in Newton-meters (Nm)
- Left Diagram Torque required to lift weight = $20 \times 0.1 = 2 \text{ Nm}$
- Right Diagram A larger Torque is required to lift the same weight since the pulley is larger.



52



Example

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

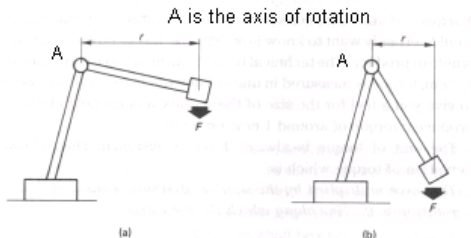- Torque exerted on a robot motor as the arm is moved about



The torque decreases as the load moves inwards towards the axis of the motor

31

52



Speed

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

32

- The speed (R) of a motor is measured in revolutions per minute (RPM). It is the link between Power(P) and Torque(T).

$$T = 10 \frac{P}{R} \text{ Newton Metres}$$

- where P is in Watts and R is in revolutions per second

52



Types of electric motors

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

33

AC motors Operated by alternating current electricity.
DC motors Operated by direct current electricity.
Stepper motor Operated by pulses of electricity



Principle of a DC motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion

Computers


DC motors

DC motor loading

Stepper motor

34

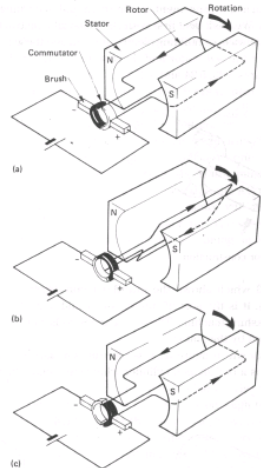- Current is led into the coil through the brushes which are held in contact with the commutator by springs.
- The current in the coil produces a magnet field which repels the magnet field of the stator (permanent magnet) and causes the coil to rotate in the direction shown by the arrow.
- The commutator shown has only 2 segments. In practice, several segments with corresponding coils can be used.



52



Relationship between Torque and armature current

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

35

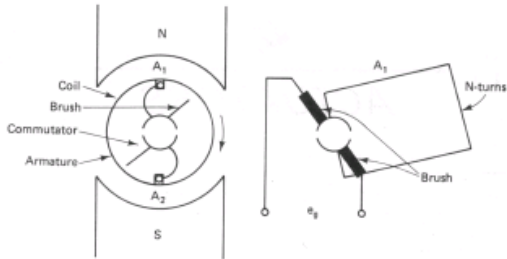

$$T = K_t \phi_F I_a$$

- T = Torque, K_t = a constant, ϕ_F = Flux of magnetic field and I_a = armature current (i.e. current in coil)

52



Current is supplied by a separate source to the field winding

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

36

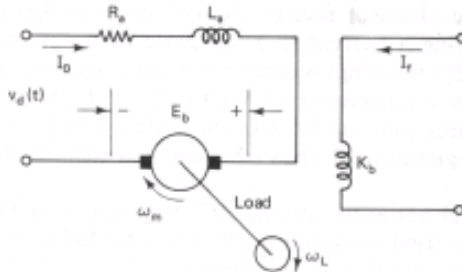

$$T = K_t K_f I_f I_a$$

- K_t , K_f are constants, I_a and I_f are armature current and field currents. K_f depends on the permeability of the iron used, Generating an electromagnet field instead of permanent magnet field

52



Categorising motors by their field windings

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion

Computers

DC motors

DC motor loading

Stepper motor

37

- Series wound motor
- Shunt wound motor
- Compound wound motor
- Permanent magnetic field

52



Series wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

38

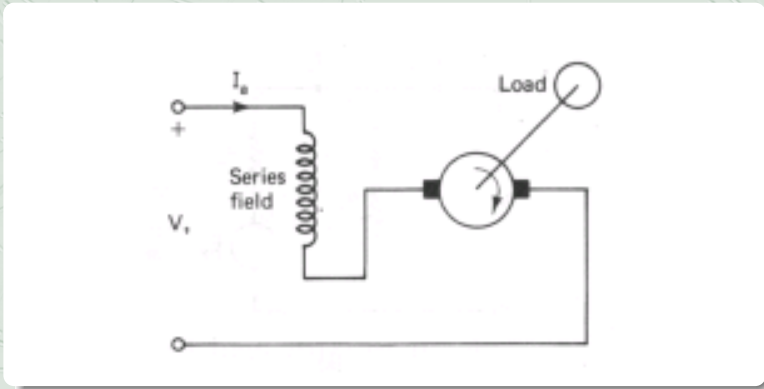

$$T = K_t K_f I_a^2$$

52



Characteristics of a series wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

39

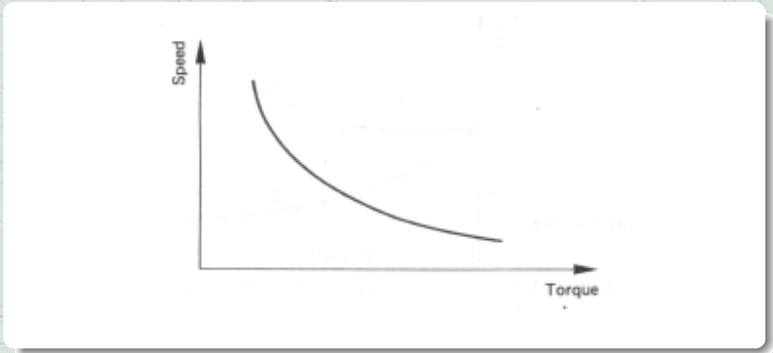

- Speed versus Torque

52



Compound wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

40

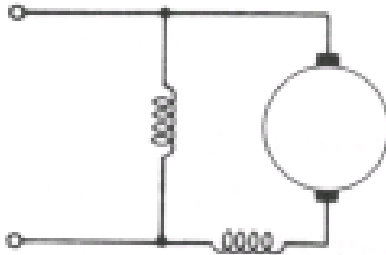

- A) Motor can be differentially compounded
- B) Commutatively compounded



Characteristics of compound wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

41

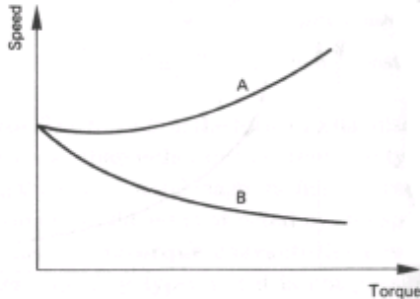

- Speed versus Torque
- Note that differentially wound motors can attain dangerous speeds if the maximum load is exceeded.



Shunt wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

42

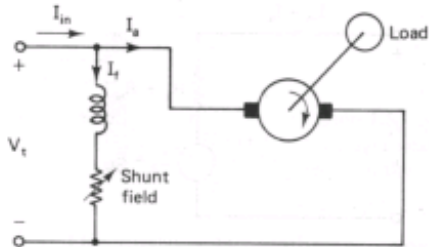

- If voltage V_t is held constant then the torque varies linearly as with the armature current I_a .

52



Characteristics of shunt wound motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

43

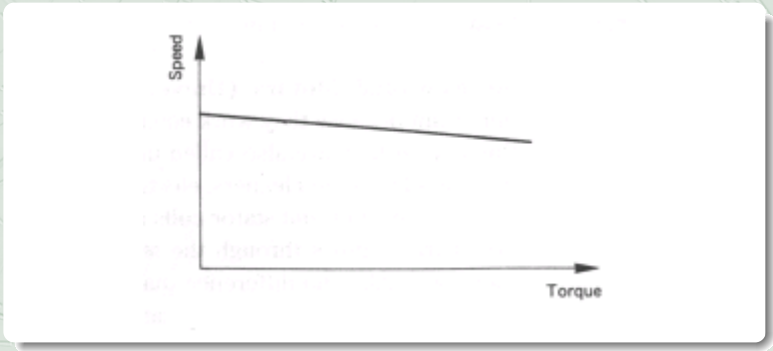

- As speed reduces torque increases



Permanent magnet motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

44

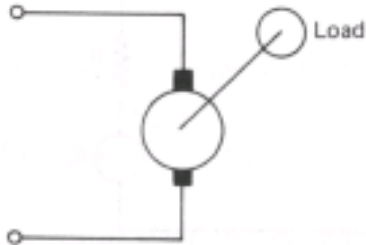

$$T = K_{pm} I_a$$

- Used mainly for servo motors. K_{pm} is the field constant and I_a is the armature current

52



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

45

DC MOTOR LOADING

52



Load on a DC motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

46

- Primary loads on motors are: Friction, Inertia, and constant or varying Torque loads.
- A rotating system in the absence of outside forces obeys:
 - $T = J\ddot{\theta} + F\dot{\theta}$ where
 - $T =$ Torque
 - $\theta =$ angular position
 - $\dot{\theta} =$ angular velocity
 - $\ddot{\theta} =$ angular acceleration



Load on a DC motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion

Computers

DC motors

DC motor loading

Stepper motor


47

- DC motors have high rotational velocities but low torque. Therefore, gearing is needed to increase torque and reduce motor speed.

- Assume a gear ratio N then,

$$T_{\text{applied to load}} = NT_{\text{applied to motor}}$$
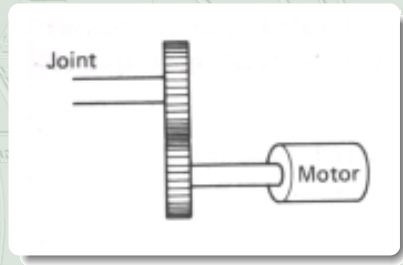
$$\dot{\theta}_{\text{load}} = \frac{1}{N} \dot{\theta}_{\text{motor}}$$



52



Load on a DC motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

48

- The load is divided by the square of the gear ratio. Therefore, the equivalent inertia J_{eq} and the equivalent friction F_{eq} seen by the motor are given by:

$$J_{eq} = J_a + \frac{1}{N^2} J_l$$

$$F_{eq} = F_a + \frac{1}{N^2} F_l$$

- J_a and F_a are the inertia and friction of the motor
- J_l and F_l are the inertia and friction of the load

52



Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

49

STEPPER MOTOR

52



Stepper Motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion

Computers

DC motors

DC motor loading

Stepper motor

50

- Operate on pulses.
- Each time a pulse is sent to the controller the motor steps (i.e rotates by a small angle),
- The angle of rotation can be from 1.5 to 30 degrees.
- Can be made to rotate faster or slower by sending more or fewer pulses.
- Computer controlled.

52



Torque-Speed characteristics

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue
conversion

Analogue to digital
conversion


Computers

DC motors

DC motor loading

Stepper motor

51

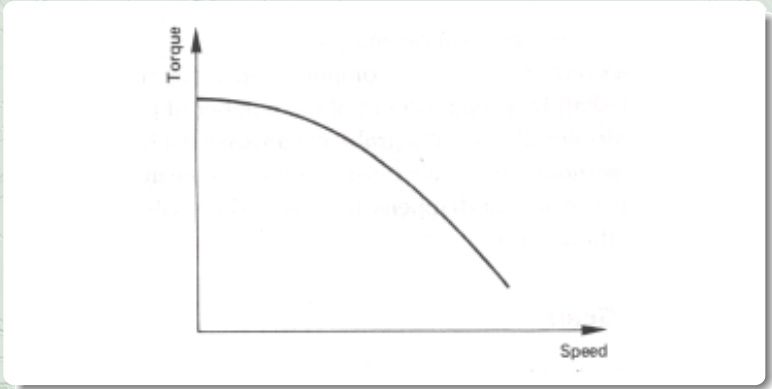

- Torque versus speed

52



Computer control of a stepper motor

Mechatronics

David Goodwin

Digital signals

Information encoding

Digital to analogue conversion

Analogue to digital conversion


Computers

DC motors

DC motor loading

Stepper motor

52

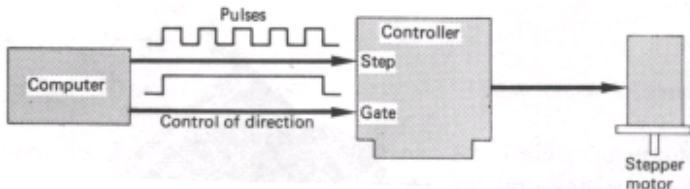

- Controlling a stepper motor

52